



Design Example Report

Title	<i>3.3W Non-isolated Flyback converter using DPA423R in 1" x 1" x 0.5"</i>
Specification	Input: -36VDC to -72VDC Output: 3.3V/1A
Application	Telecom
Author	Power Integrations Applications Department
Document Number	DER-30
Date	March 30, 2004
Revision	1.0

Summary and Features

This report details the design of a flyback converter for bias power supply of hot swap controller unit in switch network system.

- Uses DPA423R
- Non isolated -48VDC input
- No opto coupler
- 1" X 1" board space and 0.5" max component height
- Low Parts Count
- Integrated fault protection including short circuit
- Ceramic output capacitors used for higher reliability

The products and applications illustrated herein (including circuits external to the products and transformer construction) may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at www.powerint.com.

Table Of Contents

- 1 Introduction 3
- 2 Power Supply Specification..... 4
- 3 Schematic 5
- 4 Circuit Description 6
 - 4.1 Primaryside Circuit..... 7
 - 4.2 Output Rectification..... 7
 - 4.3 Output Feedback 7
- 5 PCB Layout..... 7
- 6 Bill Of Materials 8
- 7 Transformer Specification 9
 - 7.1 Electrical Diagram 9
 - 7.2 Electrical Specifications 9
 - 7.3 Transformer Construction 10
 - 7.4 Winding Instructions..... 10
 - 7.5 Materials 11
- 8 Transformer Spreadsheet 12
- 9 Performance Data 14
 - 9.1 Efficiency and Regulation..... 14
- 10 Waveforms 15
 - 10.1 Drain Voltage waveforms..... 15
 - 10.2 Start-up voltage waveform 18
 - 10.3 Output Ripple Measurements 18
 - 10.3.1 Ripple Measurement Technique 18
 - 10.3.2 Measurement Results 20
- 11 Revision History..... 22

Important Notes:

Although this board is designed to satisfy safety isolation requirements, the engineering prototype has not been agency approved. Therefore, all testing should be performed using an isolated source to provide power to the prototype board.


Design Reports contain a power supply design specification, schematic, bill of materials, and transformer documentation. Performance data and typical operation characteristics are included. Typically only a single prototype has been built.




1 Introduction

This document is an engineering report describing a non-isolated single output 3.3W, -48VDC input flyback power supply using DPA423R for bias power supply.

 The document contains the power supply specification, schematic, bill of materials, transformer documentation, printed circuit layout, and performance data.



Top view

 

Bottom View

Figure 1 – Populated Circuit Board

2 Power Supply Specification

Description	Symbol	Min	Typ	Max	Units	Comment
Input Voltage	V_{IN}	-36	-48	-72	VDC	
Output Output Voltage 1	V_{OUT1}	3.15	3.3	3.45	V	± 5%
Output Ripple Voltage 1	$V_{RIPPLE1}$			50	mV	20 MHz Bandwidth
Output Current 1	I_{OUT1}			1	A	90VSC, maximum load
Efficiency	η	65			%	Measured at P_{OUT} , 25 °C
Ambient Temperature	T_{AMB}			40	°C	Free convection, sea level



3 Schematic

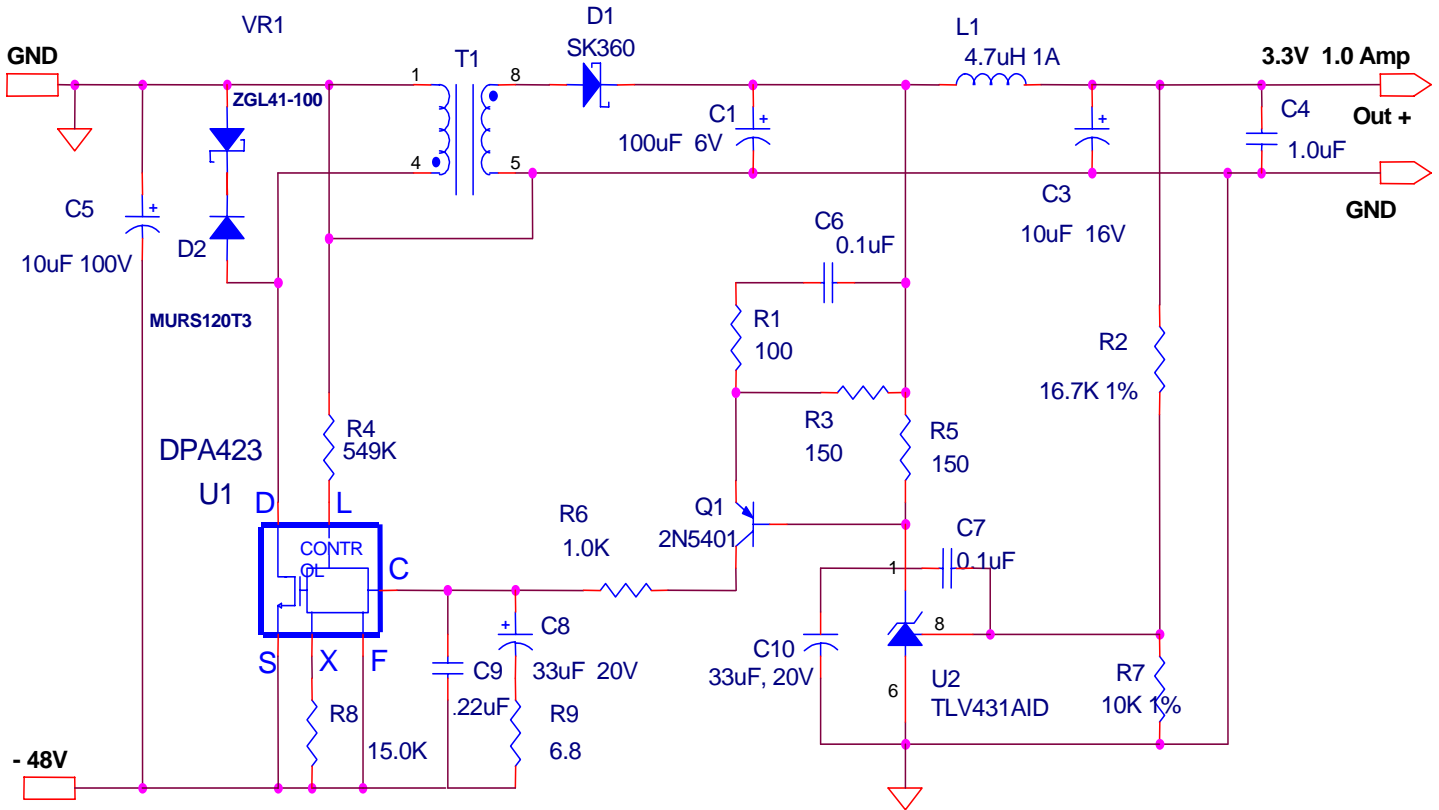


Figure 2 – Schematic



4 Circuit Description

The schematic in Figure 2 shows a non-isolated 3.3W flyback converter using DPA423R. The circuit is nominally designed for -48VDC input, 3.3V @ 1.0A output

4.1 Primary Side Circuit

The circuit is designed for -36 V to -72 Vdc input range and provides a non-isolated single 3.3V @ 1A output. C5 provides input filtering. The DC rail is applied to the primary winding of T1. The other side of the transformer primary is driven by the integrated MOSFET in U1. D2 and VR1 clamp the maximum voltage transients at the Drain of U1 caused by energy stored in the leakage inductance of the transformer.

R4 is used to set the low line turn-on threshold to approximately 33 V, and also sets the over-voltage shutdown level to approximately 88 V. C9 bypasses the U1 control pin, and provides the peak current necessary for driving the **DPA-Switch** internal MOSFET. C8 has three functions. It provides the energy required by U1 during startup, sets the auto-restart frequency during fault conditions, and also reduces the gain of U1 as a function of frequency. R9 adds a zero to stabilize the power supply control loop.

4.2 Output Rectification

The output of T1 is rectified and filtered by D1 and C1. The inductor L1, C3, and C4 provide additional high frequency filtering for the 3.3V output.


4.3 Output Feedback

Resistors R2 and R7 divide down the supply output voltage and apply it to the reference pin of the 1.25V low voltage programmable shunt regulator U2. The shunt regulator U2 drives PNP transistor Q1 to provide feedback information to the U1 control pin. Components C6, C7, C8, R1, R3, R5, and R9 all assist in compensating the power supply control loop. Capacitor C8 rolls off the gain of U1 at relatively low frequency. Resistor R9 provides a zero to cancel the phase shift of C8. Resistor R3 sets the gain of the direct signal path from the supply output through Q1 and U2. Capacitor C7 rolls off the gain of U2.



5 PCB Layout

TOP Layer

 

Bottom Layer

 


Figure 3 – Printed Circuit Layout




6 Bill Of Materials

Item	Quantity	Reference	Part	Manufacturer
1	1	C1	100uF 10V	Kemet
2	1	C3	10uF 16V	kemet
3	1	C4	1.0uF ceramic	AVX
4	1	C5	10uF 100V	UCC
5	2	C6,C7	0.1uF ceramic	AVX
6	1	C8	33uF 20V	Kemet
7	1	C9	.22uF ceramic	AVX
8	1	C10	33uF, 20V	Kemet
9	1	D1	SK360	Diode inc
10	1	D2	MURS120T3	General semi
11	1	L1	4.7uH 1A	Delta
12	1	Q1	2N5401	On semi
13	1	R1	100	Panasonic
14	1	R2	16.7K 1%	Panasonic
15	2	R3,R5	150	Panasonic
16	1	R4	549K	Panasonic
17	1	R6	1.0K	Panasonic
18	1	R7	10K 1%	Panasonic
19	1	R8	15.0K	Panasonic
20	1	T1	ER11	Delta
21	1	U1	DPA423	Power Integrations
22	1	U2	TLV431AID	National Semi
23	1	VR1	ZGL41-100	Diode inc



7 Transformer Specification

7.1 Electrical Diagram

 


7.2 Electrical Specifications

Primary Inductance (At 400KHz)	Between Pins 1 - 4 All windings open	74 uH (+/- 5%)
Resonant Frequency	All windings open	1 MHz (Min.)
Primary Leakage Inductance (At 400KHz)	Between pin 5-8 shorted	<3.0uH



7.3 Transformer construction

 

7.4 Winding Instructions

1/2 Primary Layer	Start at Pin 4. Wind 9 turns of item [3] from left to right. Finish on Pin 2.
Basic Insulation	1 Layer of tape [5] for basic insulation.
Secondary Winding	Start at Pin 8. Wind 2 bifilar turns of item [4] from left to right. Finish on Pin 5.
Basic Insulation	1 Layer of tape [5] for basic insulation.
1/2 Primary Layer	Start at Pin 2. Wind 9 turns of item [3] from left to right. Finish on Pin 1.
Final Assembly	Assemble and secure core halves. Impregnate uniformly [6].



7.5 Materials

Item	<i>Description</i>
[1]	Core: ER11-3F3
[2]	Bobbin: 8 pin ER11 surface
[3]	Magnet Wire: #30 AWG Heavy Nyleze
[4]	Magnet Wire: #28 AWG Heavy Nyleze
[5]	Tape: 3M 1298 Polyester Film
[6]	Varnish



8 Transformer Spreadsheet

	A	B	D	F	G	I
1	DAPSwitch_Flyback 090302 rev1e; Copyright Power Integrations Inc. 2002	INPUT	INFO	OUTPUT	UNITS	DPASwitch_Flyback_090302 - Continuous/Discontinuous mode Spreadsheet. Copyright 2002 Power Integrations
2	ENTER APPLICATION VARIABLES					Description
3	VDCMIN	36.00			Volts	Minimum DC Input Voltage
4	VDCMAX	72.00			Volts	Maximum DC Input Voltage
5	VO	3.30			Volts	Output Voltage
6	PO	3.30			Watts	Output Power
7	n	0.70				Efficiency Estimate
8	Z			0.70		Loss Allocation Factor, (0.7 Recommended)
9	VB	12.00			Volts	Bias Voltage (Recommended between 12V and 18V)
10						
11	UV AND OV PARAMETERS					
12			min	max		
13	VUVOFF		29.34	32.36	Volts	Minimum undervoltage On-Off threshold
14	VUVON		31.45	33.86	Volts	Maximum undervoltage Off-On threshold (turn-on)
15	VOVON		73.07	-	Volts	Minimum overvoltage Off-On threshold
16	VOVOFF			92.37	Volts	Maximum overvoltage On-Off threshold (turn-off)
17	RL			603.15	k-Ohms	
18						
19	ENTER DPASWITCH VARIABLES					
20	DPASWITCH	dpa423			16VDC	36VDC
21	Chosen Device	DPA423		Power Out	7.5W	18W
22	ILIMITMAX	1.16	1.34		Amps	From DPASWITCH Data Sheet
23	Frequency	F				Enter 'F' for fS = 400KHz and 'L' for fS = 300KHz
24	fS	400000.00			Hertz	DPASWITCH Switching Frequency
25	VOR	35.00		35.00	Volts	Reflected Output Voltage
26	KI	0.70		0.70		Current Limit Reduction Factor
27	ILIMITEXT			0.81	Amps	Minimum External Current limit
28	RX			11.00	k-Ohms	Resistor from X pin to source to set external current limit
29	VDS	2.50			Volts	DPASWITCH on-state Drain to Source Voltage
30	VD	0.50			Volts	Output Winding Diode Forward Voltage Drop
31	VDB	0.70			Volts	Bias Winding Diode Forward Voltage Drop
32	KRP/KDP	1.10				Ripple to Peak Current Ratio (0.2 < KRP < 1.0 : 1.0 < KDP < 6.0)
33						
34	ENTER TRANSFORMER CORE/CONSTRUCTION VARIABLES					
35	Core Type	ER11				
36	Core Manuf					
37	Bobbin Manuf					
38	Core		ER11		P/N:	ER11-3F3-S
39	Bobbin		ER11_Bobbin		P/N:	*
40	AE			0.12	cm^2	Core Effective Cross Sectional Area
41	LE			1.47	cm	Core Effective Path Length
42	AL			1200.00	nH/T^2	Ungapped Core Effective Inductance
43	BW			1.85	mm	Bobbin Physical Winding Width
44	M	0.00			mm	Safety Margin Width (Half the Primary to Secondary Creepage Distance)
45	L	2.00				Number of Primary Layers
46	NS	2.00				Number of Secondary Turns
47						
48	CURRENT WAVEFORM SHAPE PARAMETERS					
49	DMAX			0.49		Maximum Duty Cycle
50	Iavg			0.13	Amps	Average Primary Current
51	IP			0.54	Amps	Peak Primary Current
52	IR			0.54	Amps	Primary Ripple Current
53	IRMS			0.22	Amps	Primary RMS Current



	A	B	D	F	G	I
55	TRANSFORMER PRIMARY DESIGN PARAMETERS					
56	LP			74.20	uHenries	Primary Inductance
57	NP			18.42		Primary Winding Number of Turns
58	NB			6.68		Bias Winding Number of Turns
59	ALG			218.67	nH/T ²	Gapped Core Effective Inductance
60	BP			2748.64	Gauss	Peak Flux density exceeds 4000 Gauss. Increase NS, Increase VOR
61	BM		Warning	1819.97	Gauss	Peak Flux density<2000 Gauss, A smaller core may be used
62	BAC		Warning	909.98	Gauss	Limit AC Flux Density to less than 650 Gauss for limiting Core losses, Reduce BM, Reduce VOR
63	ur			1179.62		Relative Permeability of Ungapped Core
64	LG			0.06	mm	Gap Length (Lg >> 0.051 mm)
65	BWE			3.70	mm	Effective Bobbin Width
66						
67	TRANSFORMER SECONDARY DESIGN PARAMETERS					
68	ISP			4.95	Amps	Peak Secondary Current
69	ISRMS			1.95	Amps	Secondary RMS Current
70	IO			1.00	Amps	Power Supply Output Current
71	IRIPPLE			1.68	Amps	Output Capacitor RMS Ripple Current
72						
73	VOLTAGE STRESS PARAMETERS					
74	VDRAIN			165.50	Volts	Maximum Drain Voltage (Includes Effect of Leakage Inductance)
75	PIVS			11.12	Volts	Output Rectifier Maximum Peak Inverse Voltage
76	PIVB			38.13	Volts	Bias Rectifier Maximum Peak Inverse Voltage



9 Performance Data

All measurements unless otherwise stated performed at room temperature, 60 Hz input frequency.

9.1 Power Efficiency:


	Input Voltage (V)	Input Current (A)	Output Voltage (V)	Output current (A)	Pin (W)	Pout (W)	Efficiency (%)
No Load	-36	0.009	3.32	0	0.32		
	-48	0.008	3.32	0	0.38		
	-72	0.007	3.32	0	0.50		
Full load	-36	0.12	3.32	1	4.32	3.32	77%
	-48	0.095	3.32	1	4.56	3.32	73%
	-72	0.065	3.32	1	4.68	3.32	71%



10 Waveforms

10.1 Drain Voltage waveforms

16-Jun-03
11:03:57

 

Drain to Source voltage waveform at Vin=36VDC, Vout =3.3V @ 1A



16-Jun-03
11:03:23


HARDCOPY

output to
 Int. Printer
 File
 GPIB
 RS232
 Centronics

page feed
 OFF On

protocol
 HP 7470
 HP 7550
 TIFF b/w
 TIFF compr.
 BMP

3
 1 μ s
 50 V

 

3

- | | | | |
|----------|-----------|-------------|--------------|
| | 1 μ s | BWL | |
| 1 | .5 V | DC | $\times 100$ |
| 2 | 5 V | DC | $\times 10$ |
| 3 | 5 V | DC | $\times 10$ |
| 4 | 10 mV | 50 Ω | |

3 DC 18 V

500 MS/s


AUTO

Drain to Source voltage waveform at Vin=72VDC, Vout =3.3V @ 1A



10.2 Start up voltage waveform

6-Feb-03
18:23:50

 

3.3V output start up voltage waveform at Vin = 48VDC, Load =3 ohms



10.3 Output Ripple Measurements

10.3.1 Ripple Measurement Technique

For DC output ripple measurements, a modified oscilloscope test probe must be utilized in order to reduce spurious signals due to pickup. Details of the probe modification are provided in Figure 4.


 


Figure 4 - Oscilloscope Probe Prepared for Ripple Measurement.
(End Cap and Ground Lead Removed)

10.3.2 Measurement Results

16-Jun-03
11:10:09

TRIGGER SETUP

 


3.3V ripple voltage waveform at -36VDC input and 1A loaded output



16-Jun-03
11:10:27

TRIGGER SETUP

3
5 μ s
50 mV

 

Edge SMART

trigger on
1 2 3 4 Ext
Ext10 Line

coupling 3
DC AC LFREJ
HFREJ HF

slope 3
Pos Neg

holdoff
- - -
OFF Time Evts

500 MS/s

AUTO

- | | |
|-----------|-----------------|
| 5 μ s | BWL |
| 1 .5 V | DC $\times 100$ |
| 2 5 V | DC $\times 10$ |
| 3 5 mV | AC $\times 10$ |
| 4 10 mV | 50 Ω |



3 DC 6 mV

3.3V ripple voltage waveform at -48VDC input and 1A loaded output




16-Jun-03
11:10:44

Screen Dump stored to D003.TIF on DL-MISC of Flpy

TRIGGER SETUP

3
5 μ s
50 mV

 

Edge SMART

trigger on
1 2 3 4 Ext
Ext10 Line

coupling 3
DC AC LFREJ
HFREJ HF

slope 3
Pos Neg

holdoff
- - -
OFF Time Evt

5 μ s BWL

- 1 .5 V DC $\times 100$
- 2 5 V DC $\times 10$
- 3 5 mV AC $\times 10$
- 4 10 mV 50 Ω



3 DC 6 mV

500 MS/s

AUTO

3.3V ripple voltage waveform at -72VDC input and 1A loaded output



11 Revision History

Date	Author	Revision	Description & changes	Reviewed
March 30, 2004	DK	1.0	Initial release	VC / AM



Notes

For the latest updates, visit our Web site: www.powerint.com

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein, nor does it convey any license under its patent rights or the rights of others.

The products and applications illustrated herein (including circuits external to the products and transformer construction) may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at www.powerint.com.

The PI Logo, **TOPSwitch**, **TinySwitch**, **LinkSwitch**, and **EcoSmart** are registered trademarks of Power Integrations, Inc. **PI Expert** and **DPA-Switch** are trademarks of Power Integrations, Inc.
© Copyright 2003, Power Integrations, Inc.

WORLD HEADQUARTERS NORTH AMERICA - WEST

Power Integrations, Inc.
5245 Hellyer Avenue
San Jose, CA 95138 USA.
Main: +1-408-414-9200
Customer Service:
Phone: +1-408-414-9665
Fax: +1-408-414-9765
e-mail:
usasales@powerint.com

CHINA

Power Integrations
International Holdings, Inc.
Rm# 1705, Bao Hua Bldg.
1016 Hua Qiang Bei Lu
Shenzhen Guangdong,
518031
Phone: +86-755-8367-5143
Fax: +86-755-8377-9610
e-mail:
chinasales@powerint.com

APPLICATIONS HOTLINE

World Wide +1-408-414-9660

EUROPE & AFRICA

Power Integrations (Europe) Ltd.
Centennial Court
Easthampstead Road
Bracknell
Berkshire RG12 1YQ,
United Kingdom
Phone: +44-1344-462-300
Fax: +44-1344-311-732
e-mail: eurosales@powerint.com

KOREA

Power Integrations
International Holdings, Inc.
Rm# 402, Handuk Building,
649-4 Yeoksam-Dong,
Kangnam-Gu,
Seoul, Korea
Phone: +82-2-568-7520
Fax: +82-2-568-7474
e-mail: koreasales@powerint.com

APPLICATIONS FAX

World Wide +1-408-414-9760

SINGAPORE

Power Integrations, Singapore
51 Goldhill Plaza #16-05
Republic of Singapore,
308900
Phone: +65-6358-2160
Fax: +65-6358-2015
e-mail:
singaporesales@powerint.com

JAPAN

Power Integrations, K.K.
Keihin-Tatemono 1st Bldg.
12-20 Shin-Yokohama
2-Chome,
Kohoku-ku, Yokohama-shi,
Kanagawa 222-0033, Japan
Phone: +81-45-471-1021
Fax: +81-45-471-3717
e-mail:
japansales@powerint.com

TAIWAN

Power Integrations
International Holdings, Inc.
17F-3, No. 510
Chung Hsiao E. Rd.,
Sec. 5,
Taipei, Taiwan 110, R.O.C.
Phone: +886-2-2727-1221
Fax: +886-2-2727-1223
e-mail:
taiwansales@powerint.com

INDIA (Technical Support)

Innovatech
#1, 8th Main Road
Vasanthnagar
Bangalore, India 560052
Phone: +91-80-226-6023
Fax: +91-80-228-9727
e-mail:
indiasales@powerint.com

